

**31.34. Model:** Grounding does not affect a circuit's behavior.

**Visualize:** Please refer to Figure Ex31.34.

**Solve:** Because the earth has  $V_{\text{earth}} = 0 \text{ V}$ , point d has a potential of zero. In going from point d to point a, the potential increases by 9 V. Thus, point a is at a potential of 9 V. Let us calculate the current  $I$  in the circuit before calculating the potentials at points b and c. Applying Kirchhoff's loop rule, starting clockwise from point d,

$$\sum_i (\Delta V)_i = \Delta V_{9 \text{ V bat}} + \Delta V_{2 \Omega} + \Delta V_{3 \text{ V bat}} + \Delta V_{4 \Omega} = 0$$
$$\Rightarrow +9 \text{ V} - I(2 \Omega) - 3 \text{ V} - I(4 \Omega) = 0 \Rightarrow I = \frac{6 \text{ V}}{6 \Omega} = 1 \text{ A}$$

There is a drop in potential from point a to point b by an amount  $IR = (1 \text{ A})(2 \Omega) = 2 \text{ V}$ . Thus, the potential at point b is  $9 \text{ V} - 2 \text{ V} = 7 \text{ V}$ . The potential decreases from 7 V at point b to  $7 \text{ V} - 3 \text{ V} = 4 \text{ V}$  at point c. There is a further decrease in potential across the 4  $\Omega$  resistor of  $IR = (1 \text{ A})(4 \Omega) = 4 \text{ V}$ . That is, the potential of 4 V at c becomes 0 V at point d, as it must. In summary, the potentials at a, b, c, and d are 9 V, 7 V, 4 V, and 0 V.