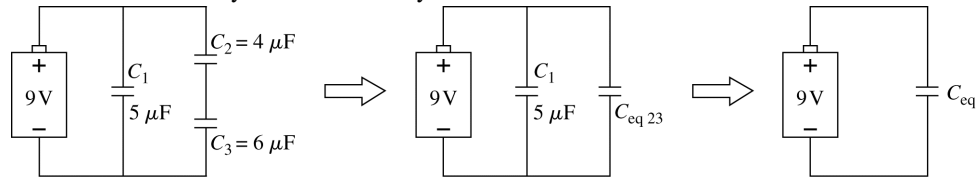


**30.65. Model:** Assume the battery is an ideal battery.

**Visualize:**



The pictorial representation shows how to find the equivalent capacitance of the three capacitors shown in the figure.

**Solve:** Because  $C_2$  and  $C_3$  are in series,

$$\frac{1}{C_{\text{eq } 23}} = \frac{1}{C_2} + \frac{1}{C_3} = \frac{1}{4 \mu\text{F}} + \frac{1}{6 \mu\text{F}} = \frac{10}{24} (\mu\text{F})^{-1} \Rightarrow C_{\text{eq } 23} = \frac{24}{10} \mu\text{F} = 2.4 \mu\text{F}$$

$C_{\text{eq } 23}$  and  $C_1$  are in parallel, so

$$C_{\text{eq}} = C_{\text{eq } 23} + C_1 = 2.4 \mu\text{F} + 5 \mu\text{F} = 7.4 \mu\text{F}$$

A potential difference of  $\Delta V_C = 9 \text{ V}$  across a capacitor of equivalent capacitance  $7.4 \mu\text{F}$  produces a charge

$$Q = C_{\text{eq}} \Delta V_C = (7.4 \mu\text{F})(9 \text{ V}) = 66.6 \mu\text{C}$$

Because  $C_{\text{eq}}$  is a parallel combination of  $C_1$  and  $C_{\text{eq } 23}$ , these capacitors have  $\Delta V_1 = \Delta V_{\text{eq } 23} = \Delta V_C = 9 \text{ V}$ . Thus the charges on these two capacitors are

$$Q_1 = (5 \mu\text{F})(9 \text{ V}) = 45 \mu\text{C} \quad Q_{\text{eq } 23} = (2.4 \mu\text{F})(9 \text{ V}) = 21.6 \mu\text{C}$$

Because  $Q_{\text{eq } 23}$  is due to a series combination of  $C_2$  and  $C_3$ ,  $Q_2 = Q_3 = 21.6 \mu\text{C}$ . This means

$$\Delta V_2 = \frac{Q_2}{C_2} = \frac{21.6 \mu\text{C}}{4 \mu\text{F}} = 5.4 \text{ V} \quad \Delta V_3 = \frac{Q_3}{C_3} = \frac{21.6 \mu\text{C}}{6 \mu\text{F}} = 3.6 \text{ V}$$

In summary,  $Q_1 = 45 \mu\text{C}$ ,  $V_1 = 9 \text{ V}$ ;  $Q_2 = 21.6 \mu\text{C}$ ,  $V_2 = 5.4 \text{ V}$ ; and  $Q_3 = 21.6 \mu\text{C}$ ,  $V_3 = 3.6 \text{ V}$ .