

31.11. Model: Assume ideal connecting wires and an ideal battery for which $\Delta V_{\text{bat}} = \mathcal{E}$.


Visualize: Please refer to Figure Ex31.11. We will choose a clockwise direction for I . Note that the choice of the current's direction is arbitrary because, with two batteries, we may not be sure of the actual current direction. The 3 V battery will be labeled 1 and the 6 V battery will be labeled 2.

Solve: (a) Kirchoff's loop law, going clockwise from the negative terminal of the 3-V battery is

$$\Delta V_{\text{closed loop}} = \sum_i (\Delta V)_i = \Delta V_{\text{bat 1}} + \Delta V_R + \Delta V_{\text{bat 2}} = 0$$

$$\Rightarrow +3 \text{ V} - (18 \Omega) I + 6 \text{ V} = 0 \Rightarrow I = \frac{9 \text{ V}}{18 \Omega} = 0.50 \text{ A}$$

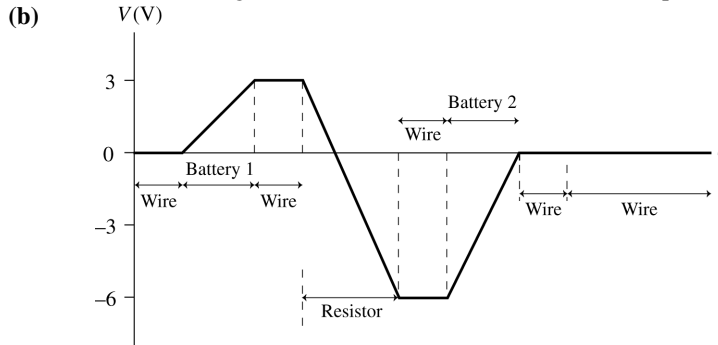Thus, the current through the 18Ω resistor is 0.50 A. Because I is positive, the current is left to right (i.e., clockwise).



Assess: The graph shows a 3 V gain in battery 1, a -9 V loss in the resistor, and a gain of 6 V in battery 2. The final potential is the same as the initial potential, as required.