

31.25. Model: Assume ideal connecting wires but not an ideal battery.

Visualize: The circuit for an ideal battery is the same as the circuit in Figure Ex31.25, except that the $1\ \Omega$ resistor is not present.

Solve: In the case of an ideal battery, we have a battery with $\mathcal{E} = 15\ \text{V}$ connected to two series resistors of $10\ \Omega$ and $20\ \Omega$ resistance. Because the equivalent resistance is $R_{\text{eq}} = 10\ \Omega + 20\ \Omega = 30\ \Omega$ and the potential difference across R_{eq} is $15\ \text{V}$, the current in the circuit is

$$I = \frac{\Delta V}{R_{\text{eq}}} = \frac{\mathcal{E}}{R_{\text{eq}}} = \frac{15\ \text{V}}{30\ \Omega} = 0.5\ \text{A}$$

The potential difference across the $20\ \Omega$ resistor is

$$\Delta V_{20} = IR = (0.5\ \text{A})(20\ \Omega) = 10\ \text{V}$$

In the case of a real battery, we have a battery with $\mathcal{E} = 15\ \text{V}$ connected to three series resistors: $10\ \Omega$, $20\ \Omega$, and an internal resistance of $1.0\ \Omega$. Now the equivalent resistance is

$$R'_{\text{eq}} = 10\ \Omega + 20\ \Omega + 1.0\ \Omega = 31\ \Omega$$

The potential difference across R_{eq} is the same as before ($\mathcal{E} = 15\ \text{V}$). Thus,

$$I' = \frac{\Delta V'}{R'_{\text{eq}}} = \frac{\mathcal{E}}{R'_{\text{eq}}} = \frac{15\ \text{V}}{31\ \Omega} = 0.4839\ \text{A}$$

Therefore, the potential difference across the $20\ \Omega$ resistor is

$$\Delta V'_{20} = I'R = (0.4839\ \text{A})(20\ \Omega) = 9.68\ \text{V}$$

That is, the potential difference across the $20\ \Omega$ resistor is reduced from $10\ \text{V}$ to $9.68\ \text{V}$ due to the internal resistance of $1\ \Omega$ of the battery. The percentage change in the potential difference is

$$\left(\frac{10\ \text{V} - 9.68\ \text{V}}{10\ \text{V}} \right) \times 100 = 3.23\%$$