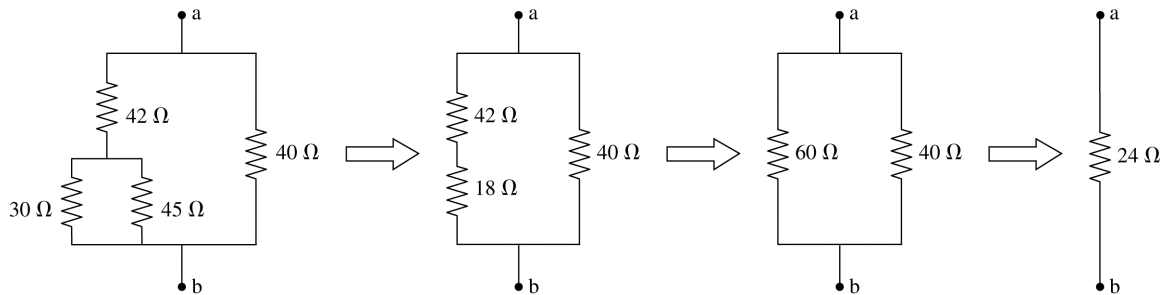


31.31. Model: The connecting wires are ideal with zero resistance.
Solve:



For the first step, the resistors $30\ \Omega$ and $45\ \Omega$ are in parallel. Their equivalent resistance is

$$\frac{1}{R_{\text{eq}_1}} = \frac{1}{30\ \Omega} + \frac{1}{45\ \Omega} \Rightarrow R_{\text{eq}_1} = 18\ \Omega$$

For the second step, resistors $42\ \Omega$ and $R_{\text{eq}_1} = 18\ \Omega$ are in series. Therefore,

$$R_{\text{eq}_2} = R_{\text{eq}_1} + 42\ \Omega = 18\ \Omega + 42\ \Omega = 60\ \Omega$$

For the third step, the resistors $40\ \Omega$ and $R_{\text{eq}_2} = 60\ \Omega$ are in parallel. So,

$$\frac{1}{R_{\text{eq}_3}} = \frac{1}{60\ \Omega} + \frac{1}{40\ \Omega} \Rightarrow R_{\text{eq}_3} = 24\ \Omega$$

The equivalent resistance of the circuit is $24\ \Omega$.