

**31.35. Model:** Grounding does not affect a circuit's behavior.

**Visualize:** Please refer to Figure Ex31.35.

**Solve:** Let us first obtain the value of the current  $I$  in the circuit. Applying Kirchhoff's loop rule, starting clockwise from point c,

$$\begin{aligned}\sum_i (\Delta V)_i &= \Delta V_{2\Omega} + \Delta V_{15\text{ V bat}} + \Delta V_{4\Omega} + \Delta V_{9\text{ V bat}} = 0 \\ \Rightarrow -I(2\Omega) + 15\text{ V} - I(4\Omega) - 9\text{ V} &= 0 \Rightarrow I = \frac{6\text{ V}}{6\Omega} = 1\text{ A}\end{aligned}$$

Because the earth has  $V_{\text{earth}} = 0\text{ V}$ , point c is at zero potential. There is a potential drop of  $IR = (1\text{ A})(2\Omega) = 2\text{ V}$  across the  $2\Omega$  resistor, so the potential at point d is  $-2\text{ V}$ . From point d to point a, there is an increase in potential of  $15\text{ V}$ , thus the potential at point a is  $15\text{ V} - 2\text{ V} = 13\text{ V}$ . The potential decreases from point a to point b by  $IR = (1\text{ A})(4\Omega) = 4\text{ V}$ , so the potential at point b is  $13\text{ V} - 4\text{ V} = 9\text{ V}$ . The potential at point c is  $9\text{ V}$  lower than the potential at b, so it  $0\text{ V}$ , as it must be. In summary, the potentials at a, b, c, and d are  $13\text{ V}$ ,  $9\text{ V}$ ,  $0\text{ V}$ , and  $-2\text{ V}$ .