

31.53. Model: Assume that the connecting wires are ideal, but the battery is not. The battery has internal resistance. Also assume that the ammeter does not have any resistance.

Visualize: Please refer to Figure P31.53.

Solve: When the switch is open,

$$\mathcal{E} - Ir - I(5.0 \, \Omega) = 0 \, \text{V} \Rightarrow \mathcal{E} = (1.636 \, \text{A})(r + 5.0 \, \Omega)$$

where we applied Kirchhoff's loop law, starting from the lower left corner. When the switch is closed, the current I comes out of the battery and splits at the junction. The current $I' = 1.565 \, \text{A}$ flows through the $5.0 \, \Omega$ resistor and the rest $(I - I')$ flows through the $10.0 \, \Omega$ resistor. Because the potential differences across the two resistors are equal,

$$I'(5.0 \, \Omega) = (I - I')(10.0 \, \Omega) \Rightarrow (1.565 \, \text{A})(5.0 \, \Omega) = (I - 1.565 \, \text{A})(10.0 \, \Omega) \Rightarrow I = 2.348 \, \text{A}$$

Applying Kirchhoff's loop law to the left loop of the closed circuit,

$$\mathcal{E} - Ir - I'(5.0 \, \Omega) = 0 \, \text{V} \Rightarrow \mathcal{E} = (2.348 \, \text{A})r + (1.565 \, \text{A})(5.0 \, \Omega) = (2.348 \, \text{A})r + 7.825 \, \text{V}$$

Combining this equation for \mathcal{E} with the equation obtained from the circuit when the switch was open,

$$(2.348 \, \text{A})r + 7.825 \, \text{V} = (1.636 \, \text{A})r + 8.18 \, \text{V} \Rightarrow (0.712 \, \text{A})r = 0.355 \, \text{V} \Rightarrow r = 0.50 \, \Omega$$

We also have $\mathcal{E} = (1.636 \, \text{A})(0.50 \, \Omega + 5.0 \, \Omega) = 9.0 \, \text{V}$.