
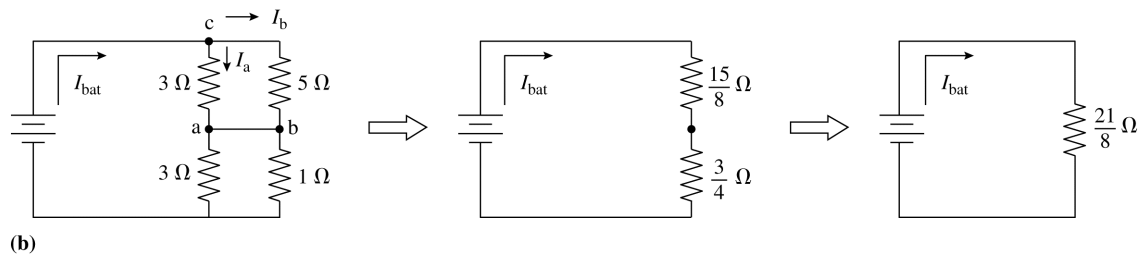


**31.63. Model:** The battery and the connecting wires are ideal.

**Visualize:**

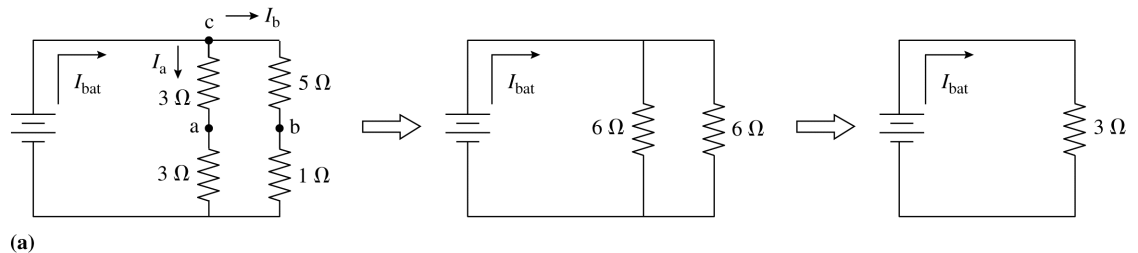

The figure shows the two circuits formed from the circuit in Figure P31.63 when the switch is open and when the switch is closed.

**Solve:** (a) Using the rules of series and parallel resistors, we have simplified the circuit in two steps as shown in figure (a). A battery with emf  $\mathcal{E} = 24 \text{ V}$  is connected to an equivalent resistor of  $3 \Omega$ . The current in this circuit is  $24 \text{ V} / 3 \Omega = 8 \text{ A}$ . Thus, the current that flows through the battery is  $I_{\text{bat}} = 8 \text{ A}$ . To determine the potential difference  $\Delta V_{ab}$ , we will find the potentials at point a and point b and then take their difference. To do this, we need the currents  $I_a$  and  $I_b$ . We note that the potential difference across the  $3 \Omega$ - $3 \Omega$  branch is the same as the potential difference across the  $5 \Omega$ - $1 \Omega$  branch. So,

$$\mathcal{E} = 24 \text{ V} = I_a(3 \Omega + 3 \Omega) \Rightarrow I_a = 4 \text{ A} = I_b$$

Now,  $V_c - I_a(3 \Omega) = V_a$ , and  $V_c - I_b(5 \Omega) = V_b$ . Subtracting these two equations give us  $\Delta V_{ab}$ :

$$V_a - V_b = I_b(5 \Omega) - I_a(3 \Omega) = (4 \text{ A})(5 \Omega) - (4 \text{ A})(3 \Omega) = +8 \text{ V}$$

(b) Using the rules of the series and the parallel resistors, we have simplified the circuit as shown in figure (b). A battery with emf  $\mathcal{E} = 24 \text{ V}$  is connected to an equivalent resistor of  $\frac{21}{8} \Omega$ . The current in this circuit is  $24 \text{ V} / \frac{21}{8} \Omega = 9.143 \text{ A}$ . Thus, the current that flows through the battery is  $I_{\text{bat}} = 9.14 \text{ A}$ . When the switch is closed, points a and b are connected by an ideal wire and must therefore be at the same potential. Thus  $V_{ab} = 0 \text{ V}$ .