

**33.21. Visualize:** Please refer to Figure Ex33.21. This is a simple  $LR$  circuit if the resistors in parallel are treated as an equivalent resistor in series with the inductor.

**Solve:** We can find the equivalent resistance from the time constant since we know the inductance. We have

$$\tau = \frac{L}{R_{\text{eq}}} \Rightarrow R_{\text{eq}} = \frac{L}{\tau} = \frac{3.6 \times 10^{-3} \text{ H}}{10 \times 10^{-6} \text{ s}} = 360 \ \Omega$$

The equivalent resistance is the parallel addition of the unknown resistor  $R$  and  $600 \ \Omega$ . We have

$$\frac{1}{R_{\text{eq}}} = \frac{1}{600 \ \Omega} + \frac{1}{R} \Rightarrow R = \frac{(600 \ \Omega)(360 \ \Omega)}{600 \ \Omega - 360 \ \Omega} = 900 \ \Omega$$