
33.61. Model: Assume we can ignore the sharp corners when the current changes abruptly.

Visualize: The changing current produces a changing flux, an induced emf, and a corresponding potential difference.

Solve: Break the current into time intervals over which the current is changing linearly or not at all. For the intervals 1 ms to 2 ms and 4 ms to 5 ms, the current does not change, so the potential difference is zero. For the interval 0 s to 1 ms, the current goes from 0 A to 1 A, so the potential difference is

$$\Delta V_{\rm L} = -L \frac{dI}{dt} = -L \frac{\Delta I}{\Delta t} \Rightarrow \Delta V_{\rm L} = -(10 \times 10^{-3} \text{ H}) \frac{1 \text{ A} - 0 \text{ A}}{(1 \text{ s} - 0 \text{ s}) \times 10^{-3}} = -10 \text{ V}$$

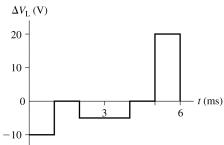Similarly for the interval 2 ms to 4 ms, the potential difference is -5 V. For the interval 5 ms to 6 ms, the potential difference is +20 V.



Assess: The potential difference is proportional to the negative slope of the current versus time graph.